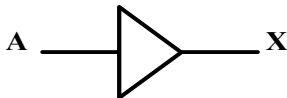
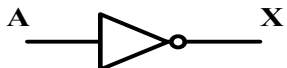
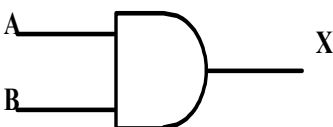
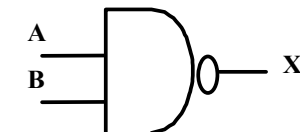
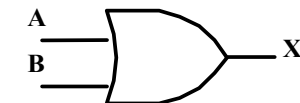
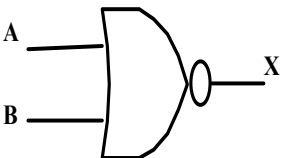

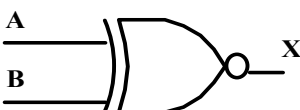


## Digital Electronics


See Boolean Algebra for a description of the category as well as references.

NAME	GRAPHICAL SYMBOL	ALGEBRAIC EQN	TRUTH TABLE															
BUFFER		$X = A$	<table><tr><td><u>A</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	<u>A</u>	<u>X</u>	0	0	1	1									
<u>A</u>	<u>X</u>																	
0	0																	
1	1																	
NOT		$X = \overline{A}$	<table><tr><td><u>A</u></td><td><u>X</u></td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	<u>A</u>	<u>X</u>	0	1	1	0									
<u>A</u>	<u>X</u>																	
0	1																	
1	0																	
AND		$X = AB \text{ or } A*B$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	0	0	1	0	1	0	0	1	1	1
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
NAND		$X = \overline{AB} \text{ or } \overline{A*B}$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	1	0	1	1	1	0	1	1	1	0
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
OR		$X = A+B$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	0	0	1	1	1	0	1	1	1	1
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOR		$X = \overline{A+B}$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	1	0	1	0	1	0	0	1	1	0
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
EXCLUSIVE-OR (XOR)		$X = A \oplus B$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	0	0	1	1	1	0	1	1	1	0
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
EQUIVALENCE (XNOR)		$X = \overline{A \oplus B}$	<table><tr><td><u>A</u></td><td><u>B</u></td><td><u>X</u></td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	<u>A</u>	<u>B</u>	<u>X</u>	0	0	1	0	1	0	1	0	0	1	1	1
<u>A</u>	<u>B</u>	<u>X</u>																
0	0	1																
0	1	0																
1	0	0																
1	1	1																
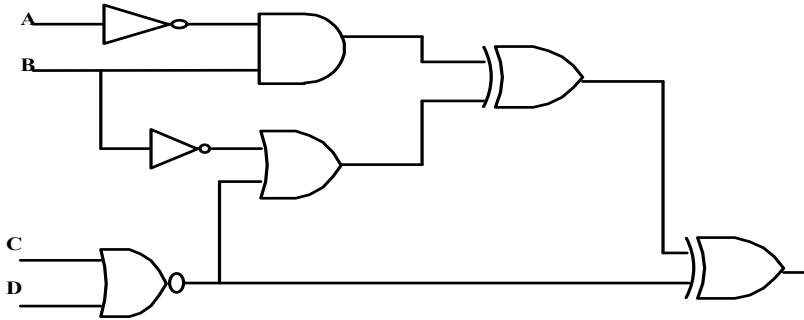
## Sample Problems

---

Find all ordered 4-tuples  $(A, B, C, D)$ , which make the following circuit **FALSE**:



The circuit translates to the following Boolean expression:

$$(\overline{C + D + B}) \oplus (\overline{A}B) \oplus (\overline{C + D})$$


The following table has the following headings: H1 is  $\overline{(C + D)}$ , H2 is  $H1 + \overline{B}$ , H3 is  $\overline{A}B$ , H4 is  $H2 \oplus H3$  and H5 is  $H4 \oplus H1$ , the final expression.

A	B	C	D	H1	H2	H3	H4	H5
0	0	0	0	1	1	0	1	0
0	0	0	1	0	1	0	1	1
0	0	1	0	0	1	0	1	1
0	0	1	1	0	1	0	1	1
0	1	0	0	1	1	1	0	1
0	1	0	1	0	0	1	1	1
0	1	1	0	0	0	1	1	1
0	1	1	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	0	0	1	0	1	1
1	0	1	1	0	1	0	1	1
1	1	0	0	1	1	0	1	0
1	1	0	1	0	0	0	0	0
1	1	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0

Thus, the 4-tuples  $(0,0,0,0)$ ,  $(1,0,0,0)$ ,  $(1,1,0,0)$ ,  $(1,1,0,1)$ ,  $(1,1,1,0)$ , and  $(1,1,1,1)$  all make the circuit **FALSE**.

---

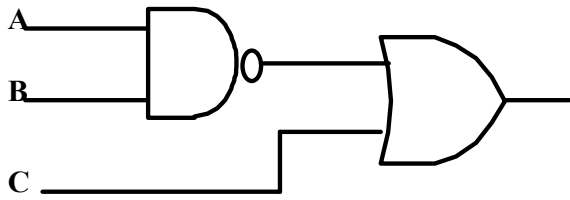Find all ordered triplets  $(A, B, C)$  which make the following circuit **FALSE**:



The circuit translates to the following Boolean expression:  $\overline{AB} + C$ . To find when this is **FALSE** we can equivalently find when the  $\overline{\overline{AB} + C}$  is **TRUE**. We can simplify this by applying DeMorgan's Law and cancelling the double *not* over  $AB$  to yield  $ABC$ . This is **TRUE** when all three terms are **TRUE**, which happens for  $(1, 1, 0)$ .